

PH3244
Experiment - 3
FET Characteristics

Aumshree P. Shah
20231059^{a)} and

Co-author: Yojit Kumar^{b)}

(Dated: 2 April 2026)

Synopsis

In this experiment we see the characteristics of a FET transistor and calculate some properties of it.

CONTENTS

I. Theory and Procedure	2
A. Theory	2
B. Procedure	2
II. Observation	3
A. For constant V_{DS}	3
B. For constant V_{GS}	3
III. Calculations, Analysis and Characteristics	3
A. Sources of Error	3
1. Systematic Errors	3
2. Random Errors	4
B. Error Propagation	4
C. Plots and Calculation	4
IV. Result and Conclusion	5
A. Checking the observed values with theoretical	5
B. Comments on how to improve the experiment	5
C. Why the first dataset was discarded	6
References	6

^{a)} aumshree.pinkalbenshah@students.iiserpune.ac.in

^{b)} 20231289_yojit.kumar@students.iiserpune.ac.in

I. THEORY AND PROCEDURE

A. Theory¹

AC Drain Resistance, r_D :

It is the AC resistance between drain and source terminals when JFET is operating in the pinch-off region. To calculate AC drain resistance calculate the slope of the drain characteristics in the pinch off region. r_D =change on V_{DS} change on I_D at V_{GS} constant or $r_D = V_{DS} / I_D$ at constant V_{GS} It has a very high value.

$$g_m = \frac{\text{change on } V_{DS}}{\text{change on } I_D} \text{ at constant } V_{GS} \text{ or}$$

$$r_D = \frac{V_{DS}}{I_D} \text{ at constant } V_{GS} \quad (1)$$

It has a very high value.

Transconductance, g_m :

To calculate transconductance determine slope of the transfer characteristics.

$$g_m = \frac{\text{change on } I_D}{\text{change on } V_{GS}} \text{ at constant } V_{GS} \quad (2)$$

Its unit is Siemens (S) / mho.

Amplification factor, μ :

It is given by

$$\mu = \frac{\text{change on } V_{DS}}{\text{change on } V_{GS}} \text{ at } I_D \text{ constant or}$$

$$\mu = \frac{V_{DS}}{V_{GS}} \text{ at constant } I_{DS}$$

$$\text{Or } \mu = g_m * r_d \quad (3)$$

DC drain resistance, R_{DS} :

It is also called the static or ohmic resistance of the channel. It is given by

$$R_{DS} = \frac{V_{DS}}{I_D} \quad (4)$$

B. Procedure

Refer to the manual [Cat (2026)] for a look at procedure, although the required pages will be attached at the back for submition along with the signed report.

¹ Please refer to [Cat (2026)] for a full examination of theory, only the important results will be discussed here.

II. OBSERVATION

A. For constant V_{DS}

V_{GS} (V)	I_D (mA)
0.000	7.17
0.197	5.78
0.397	4.41
0.604	3.17
0.807	2.14
1.000	0.98
1.199	0.64

TABLE I: $V_{DS} = -2.65V$

V_{GS} (V)	I_D (mA)
0.000	8.58
0.202	6.86
0.402	5.23
0.684	3.94
0.799	2.76
0.999	1.75
1.203	0.44

TABLE II: $V_{DS} = -5V$

B. For constant V_{GS}

V_{DS} (V)	I_{GS} (mA)
-1.05	5.53
-2.01	7.15
-3.55	7.87
-4.04	8.27
-5.08	8.59
-6.02	8.79
-7.03	9.00
-8.08	9.16
-9.02	9.30
-10.01	9.42
-11.01	9.52
-12.07	9.59
-13.04	9.79

TABLE III: $V_{GS} = 0V$

V_{DS} (V)	I_{GS} (mA)
-1.09	0.08
-1.96	0.11
-3.02	0.15
-3.97	0.17
-5.05	0.20
-6.00	0.22
-7.04	0.25
-8.45	0.27
-8.98	0.30
-10.02	0.33

TABLE IV: $V_{GS} = 1.558V$

V_{DS} (V)	I_{GS} (mA)
-1.00	1.01
-2.05	1.30
-3.14	1.51
-4.15	1.65
-5.03	1.76
-6.03	1.88
-7.12	2.00
-8.01	2.09
-9.54	2.19
-10.00	2.27
-11.10	2.37
-12.04	2.46

TABLE V: $V_{GS} = 1V$

$$V_{PO} = 2.3V.$$

The least count is to be interpreted by the number of significant digits of that column.

Data taken on 6 Feb 2026 by 20231289²

III. CALCULATIONS, ANALYSIS AND CHARACTERISTICS

A. Sources of Error

1. Systematic Errors

1. Heating of transistor
2. Resistance, Impedance and Capacitance of wiring and breadboard
3. Deviation from the actual value of resistor

² The data taken on 4 Feb 2026 is not written, for further details refer to Appendix - C.

2. Random Errors

1. Uncertainty in instruments

B. Error Propagation

To calculate the standard deviation from values we have measured with some least count, and the values we have applied digitally, we use the formula [Tewari (2016)]:

$$\sigma = \frac{\text{Least Count}}{\sqrt{12}} \quad (5)$$

and to calculate the standard deviation for values we have applied on analog instrument with some least count, we use the formula [Tewari (2016)]:

$$\sigma = \frac{\text{Least Count}}{\sqrt{24}} \quad (6)$$

Furthermore, we will calculate the uncertainty of r_D and g_m from the slope of their graph, to do that we will assume that the random error is much greater than the uncertainty calculated from Eq - 5, 6. To calculate the μ we see from Eq - 3 and from [Taylor (1997)] that:

$$\Delta\mu = \mu \sqrt{\left(\frac{\Delta g_m}{g_m}\right)^2 + \left(\frac{\Delta r_d}{r_d}\right)^2} \quad (7)$$

C. Plots and Calculation³

First since we only want to see the characteristics of the transistors, we won't be taking any errors into consideration, We plot Table I-V and see:

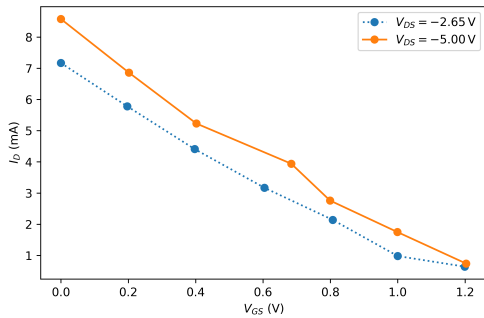


FIG. 1: I_d vs V_{GS} from Table - I, II

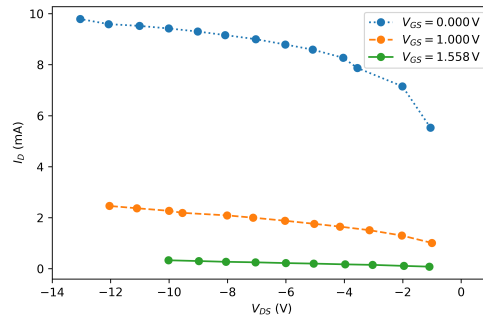


FIG. 2: I_d vs V_{DS} from Table - III, IV, V

Here we see that the characteristics of Fig - 1 is linear whereas the Fig - 2 characteristics suddenly increases from 0 to a high current and then stabilizes out.

³ Refer to [Cat (2026)] for the code used to plot and determine the slope.

Now to calculate the r_D we shall take the region before $V_{DS} = -5V$ for linear best fit and for g_m we will do a best linear fit for the entire graph. Doing a best linear fit we get:

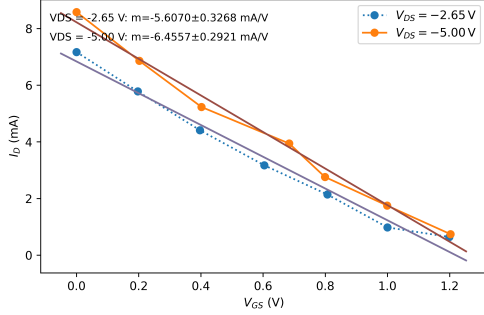


FIG. 3: Best linear fit for I_d vs V_{GS}

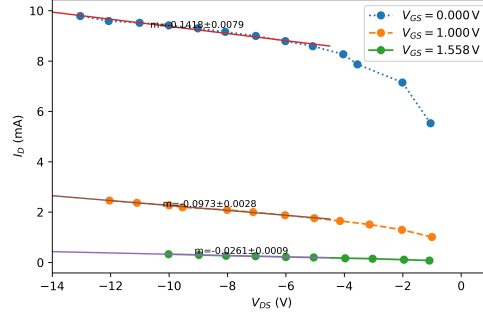


FIG. 4: Best linear fit for I_d vs V_{DS}

From this we get:

$$\begin{aligned}
 V_{GS} = 0.000V &\implies -0.141850.00786mA/V \\
 V_{GS} = 1.558V &= -0.026150.00087mA/V \\
 V_{GS} = 1.000V &= -0.097330.00276mA/V \\
 V_{DS} = -2.65V &= -5.606980.32677mA/V \\
 V_{DS} = -5.00V &= -6.455740.29215mA/V
 \end{aligned}$$

IV. RESULT AND CONCLUSION

$$\hat{p}_t = \underset{(1.958)}{0.900} + \underset{(0.017)}{0.997}p_{t-1}, \quad (8)$$

Cat (2026) Tewari (2016) Taylor (1997) sta (2026)

Appendix A: Checking the observed values with theoretical

here add the theo val adn comment if hter is any diff add tyhe 5th refarence

Appendix B: Comments on how to improve the experiment

To calculate the DC drain resistance R_{DS} , there was not enough value taken in the interval of -1 - 0. Further measurements are needed to determine it.

To reduce the error due to heating, we should take the measurement as soon as possible to make the error as low as possible.

Appendix C: Why the first dataset was discarded

The first dataset taken on 4 Feb 2026 is discarded and not written in the report as it was later found out that the FET given to us was faulty. A empty signed sheet of that date will be attached for summision.

REFERENCES

- L. M. Cat, Ph3244 3rd year sem 6 physics lab repo: <https://github.com/laughingcatmeme/ph3244> (2026).
G. M. Tewari, Measurement uncertainty, International Workshop and Training Program on Good Food Laboratory Practices (2016).
J. R. Taylor, *An Introduction to Error Analysis* (1997).
Standard error, Wikipedia (2026).